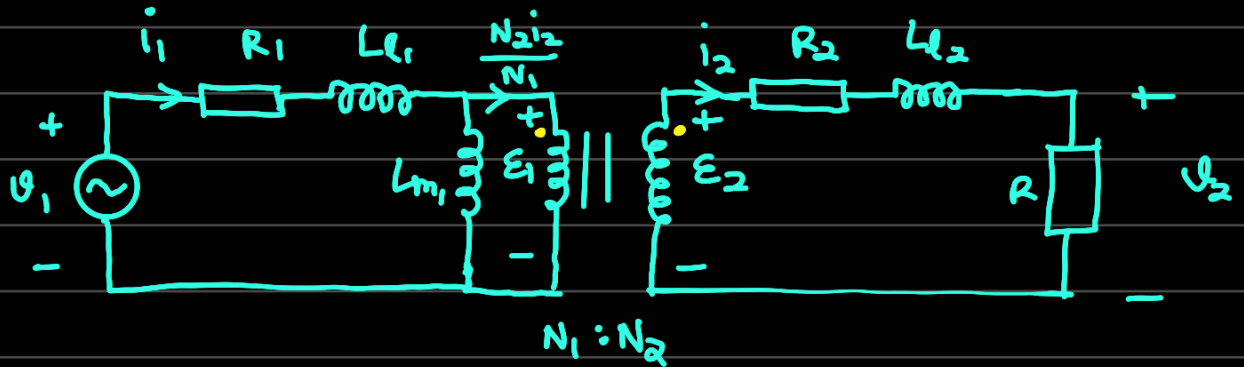


## Day - 19

→ Transformers:



Steady-state equivalent circuit of transformer.

$$\begin{aligned}\phi_1 &= N_1 \phi_1 = N_1 (\phi_L + \phi_m) \\ &= N_1 \phi_L + N_1 \phi_m\end{aligned}$$

$$= L_{e1} i_1 + N_1 \left( \frac{N_1 i_1 - N_2 i_2}{R_c} \right)$$

$$= \underbrace{\left( L_{e1} + \frac{N_1^2}{R_c} \right)}_{L_{m1}} i_1 - \frac{N_1 N_2}{R_c} i_2$$


$$= \underbrace{(L_{e1} + L_{m1})}_{\text{Self-inductance of coil 1 (L}_{11})} i_1 - \underbrace{L_{12} i_2}_{\substack{\text{mutual inductance} \\ \text{between coils 1} \\ \text{and 2.}}}$$

$$\phi_2 = (L_{e2} + L_{m2}) i_2 - L_{21} i_1$$

$$E_2 = i_2 R_2 + L_{e2} \frac{di_2}{dt} + i_2 R$$

$$\frac{N_2}{N_1} E_1 = \frac{N_1}{N_2} i_2' R_2 + L_{e2} \frac{N_1}{N_2} \frac{di_2'}{dt} + \frac{N_1}{N_2} i_2' R$$
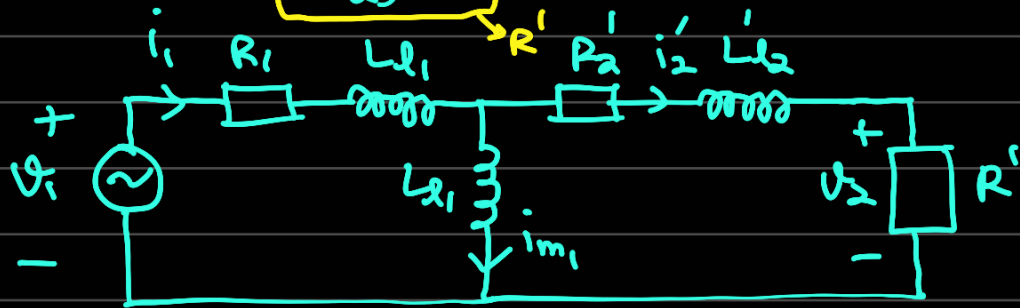
$$\Rightarrow \epsilon_1 = \underbrace{\left(\frac{N_1}{N_2}\right)^2 R_2 i_2'}_{R_2'} + \underbrace{\left(\frac{N_1}{N_2}\right)^2 L_2 \frac{di_2'}{dt}}_{L_2'} + \underbrace{\left(\frac{N_1}{N_2}\right)^2 R_1 i_2'}_{R_1'}$$




$$(i_2' = \frac{N_2 i_2}{N_1})$$

we performed power-invariant transformation

→ Open Circuit Test :

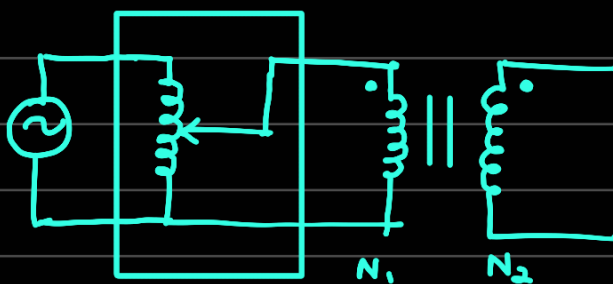secondary winding is open (the no-load case)





1 kVA  
200/100 V

Single phase  
1ph Auto-transformer

- Apply rated voltage to transformer

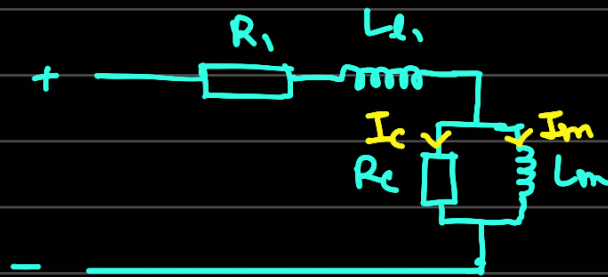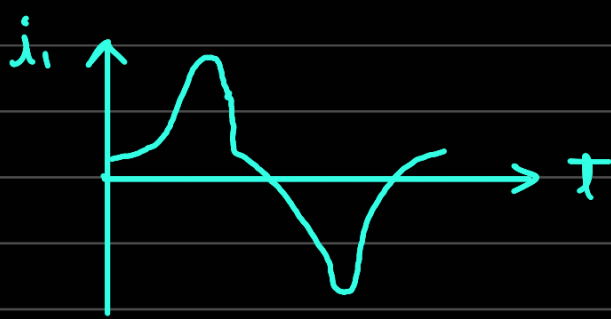we can't directly apply rated voltage to transformer → leads to flow of inrush current, which affects the lifetime of the device. That is why auto-transformer is used.



$$i_1(t) = I_c \sin \omega t + I_m \cos \omega t$$

$$v_1(t) = V_m \sin \omega t$$

[ $R_1$  and  $L_{l1}$  may be neglected]


$$R_c = \frac{V_m}{I_c}, \quad L_m = \frac{V_m}{2\pi f I_m}$$

we can calculate core loss, shunt parameter.

$$\text{Core loss (Pc)} = \frac{V_m I_c}{2}$$

Standard wire gauge (SWG)  $\uparrow \Rightarrow$  thickness  $\downarrow$

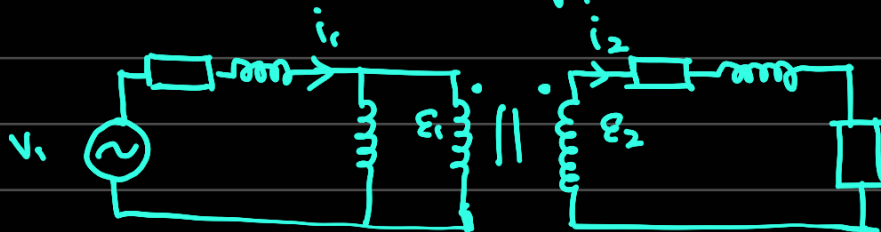☆  $i_1$  has peaky nature under no-load condition  
But when load is applied:



$V_1$  is sinusoidal  $\Rightarrow E_1$  is sinusoidal

$$(\because V_1 \approx \frac{d\psi}{dt})$$


$\Rightarrow E_2$  is sinusoidal

$\Rightarrow i_2$  is sinusoidal (only R-L components in secondary ckt.)

But  $i_1 \sim \frac{N_1}{N_2} i_2$

$\Rightarrow i_1$  is sinusoidal


→ Short-circuit Test:

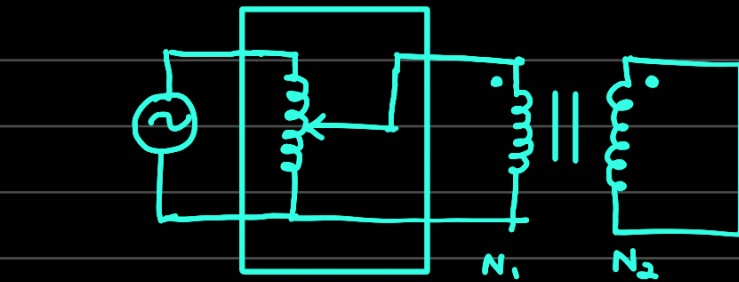

Single phase  
1ph Auto-transformer

Be careful!  
High current!  
Don't apply  
rated voltage!

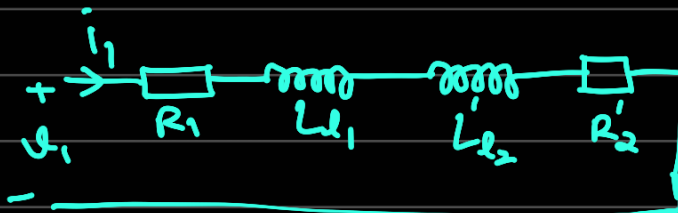- Apply low voltage so that rated current flows in the circuit.
- Since  $V_m \downarrow \Rightarrow \phi_m \downarrow \Rightarrow \text{core loss} \downarrow \Rightarrow I_{m2} \downarrow$   
no load



$$v_1(t) = V_m \sin \omega t$$

$$i_1(t) = I_1 \sin(\omega t - \theta)$$

$$= I_1 \cos \theta \sin \omega t - I_1 \sin \theta \cos \omega t$$

$$\frac{V_m \angle 0^\circ}{I_1 \angle -\theta} = R_1 + R'_2 + j(X_{L1} + X'_{L2})$$

$$\Rightarrow R_1 + R_2 = \frac{V_m}{I_1 \cos \theta}, \quad X_{L1} + X'_{L2} = \frac{V_m}{I_1 \sin \theta}$$