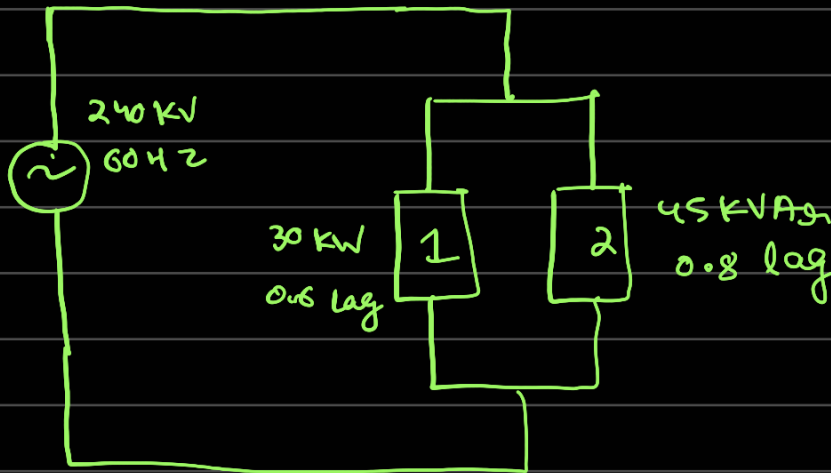


## Day - 10

- 1.) 2 balance loads are connected to a 240 kV RMS, 60 Hz line. Load 1 draws 30 kW at 0.6 power factor lagging while load 2 draws 45 kVA at 0.8 power factor lagging. Find real, reactive and apparent power absorbed by the combined load.




Ans.)

$$\begin{aligned}
 S &= \frac{30}{0.6} \angle 53^\circ + \frac{45}{0.8} \angle 37^\circ \\
 &= 50 \left( \frac{3}{5} + \frac{4j}{5} \right) + 75 \left( \frac{4}{5} + \frac{3j}{5} \right) \\
 &= 30 + 40j + 60 + 45j \\
 &= 90 + 85j \text{ kW}
 \end{aligned}$$

$\downarrow \quad \downarrow$   
 $P_{\text{total}} \quad Q_{\text{total}}$

2.)

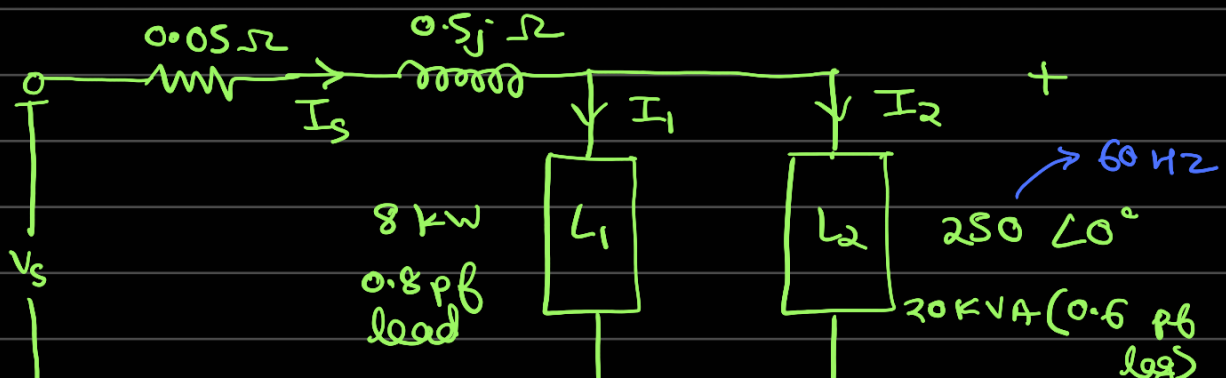

- a) Find p.f. combined of  $L_1, L_2$   
 b) Find  $I_1 + I_2$   
 c) What capacitance must be added in || to  $L_1, L_2$  to make  $p.f. = 1$ ?

Ans.) a)  $\frac{8}{0.8} \angle 37^\circ + 20 (0.6 - 0.8j)$

$$= 2(4 + 3j) - 2(6 + 8j)$$

$$= 20 - 10j \text{ kW}$$

$$p.f. = \frac{1}{\sqrt{1 + (0.5)^2}} = \frac{1}{\sqrt{1.25}} \text{ lag}$$

$$\approx 0.894$$

b)  $250 \times I_1 \times 0.8 = 8000$

$$\Rightarrow I_1 = 40 \text{ A} \quad (\text{rms})$$

$\rightarrow \angle 37^\circ$

$$250 \times I_2 \times 0.6 = 12000$$

$$\Rightarrow I_2 = 80 \angle -53^\circ$$

$$I_1 + I_2 = 8(4 + 3j) + 16(3 - 4j)$$

$$= 80 - 40j$$

c) let  $X_c$  be added.

$$\text{So } 10 \times 1000 = 250 \times 250 \times 2\pi \times 60 \times C$$





$$\Rightarrow C = \frac{10000}{250 \times 500 \times 60\pi} \text{ F}$$


$$= \frac{1}{750\pi} \text{ F}$$

$$\approx 0.424413 \text{ mF}$$


$$\approx 424.413 \mu\text{F}$$

→ 3-phase circuit:

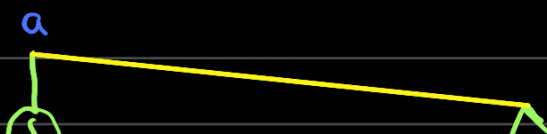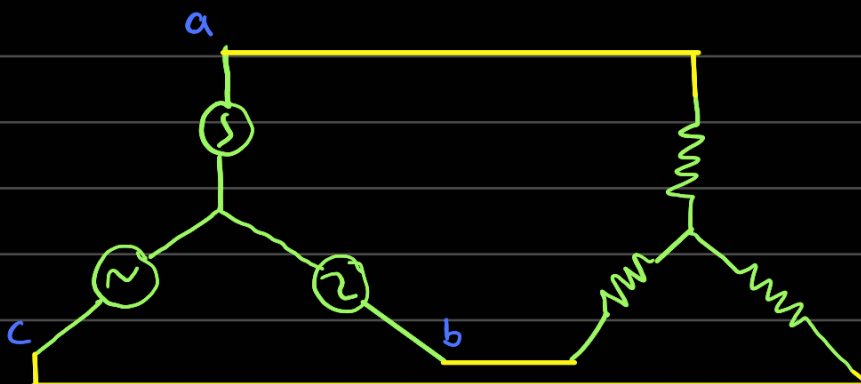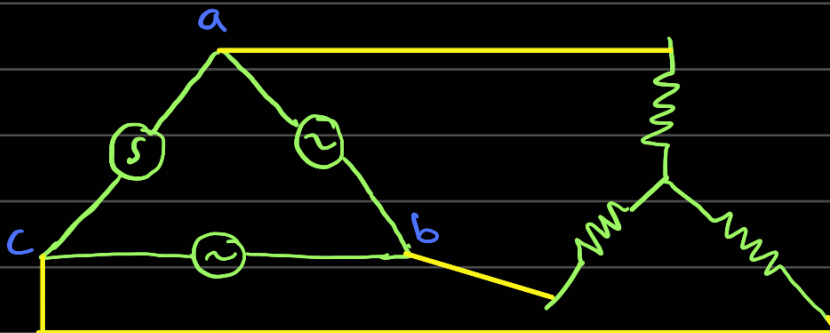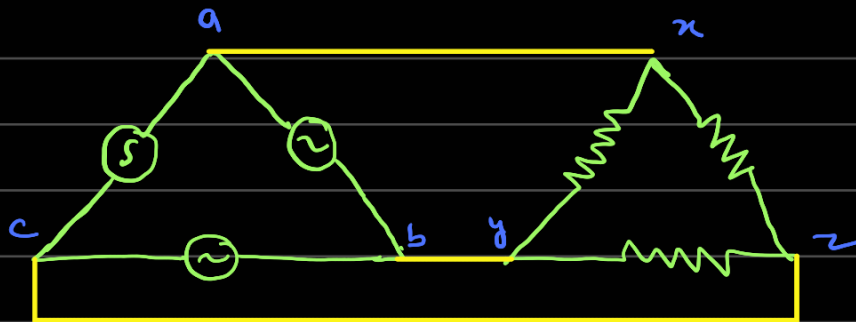

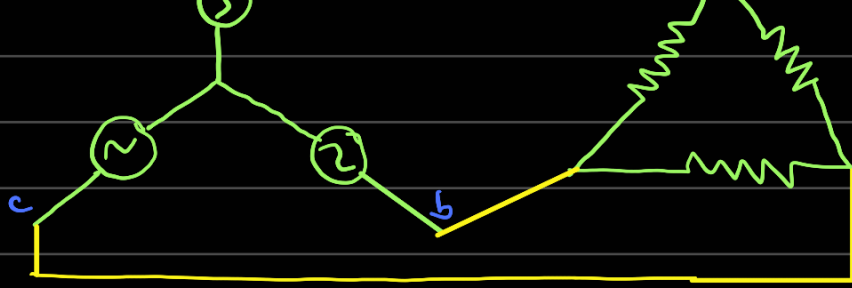

→

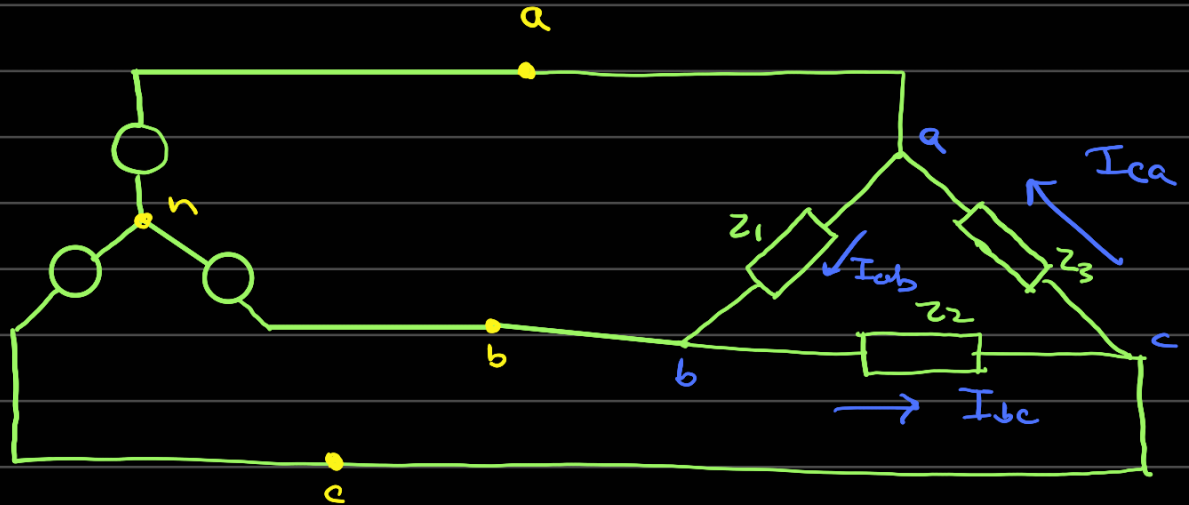

$$V_{ab} = V_{an} - V_{bn}$$

$$= V_m \cos \omega t - V_m \cos (\omega t - 2\pi/3)$$

$$= 2V_m \sin (\omega t - \pi/3) \sin (-2\pi/3)$$

$$= \sqrt{3} V_m \cos (\omega t + \pi/6)$$

$V_{an}, V_{bn}, V_{cn} \rightarrow$  phase voltage  
 $V_{ab}, V_{bc}, V_{ac} \rightarrow$  line voltage

$$V_{ab} = \sqrt{3} V_A \angle 30^\circ$$

$$V_{bc} = \sqrt{3} V_b \angle 30^\circ$$

$$V_{ca} = \sqrt{3} V_c \angle 30^\circ$$

$$I_{ab} = \frac{V_{ab}}{R_1} = \frac{\sqrt{3} V_A}{Z_1} \angle 30^\circ$$

$$I_{bc} = \frac{V_{bc}}{R_2} = \frac{\sqrt{3} V_b}{Z_2} \angle 30^\circ$$

$$I_{ca} = \frac{V_{ca}}{R_3} = \frac{\sqrt{3} V_c}{Z_3} \angle 30^\circ$$

$$I_a = \sqrt{3} I_{ab} \angle -30^\circ$$

$$I_b = \sqrt{3} I_{bc} \angle -30^\circ$$

$$I_c = \sqrt{3} I_{ca} \angle -30^\circ$$

