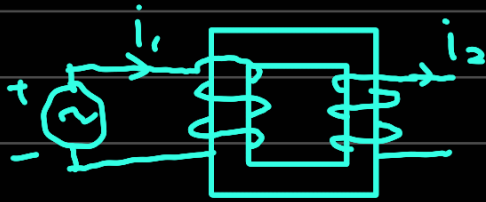


Day-17

→ Transformer: no-load operation



no load: $i_2 = 0$



$$V_1 = i_1 R_1 + \frac{d\psi}{dt}$$

neglecting resistance drop,

$$V_1 \approx \frac{d\psi}{dt} = N \frac{d\phi}{dt}$$

$$V_1 = V_m \sin \omega t \Rightarrow \phi = -\frac{V_m}{N\omega} \cos \omega t$$

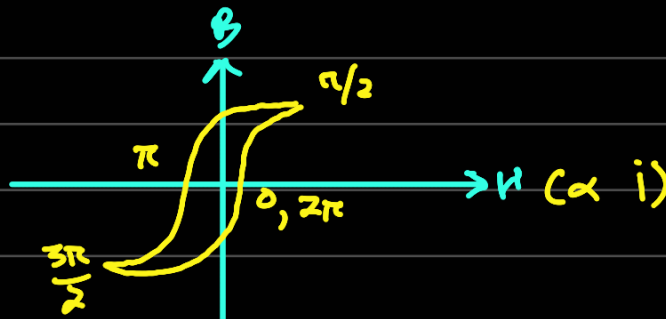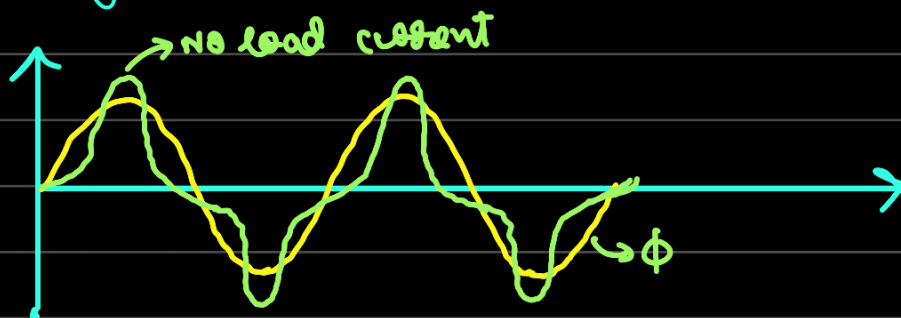⇒ No load current of a transformer is not sinusoidal, because of non-linear and multi-valued nature of B-H curve of core.



→ $i_1(t)$ has half-wave symmetry (HWS)

$$i_1(t) = -i_1(t \pm T/2)$$

$T \rightarrow$ time period of $i_1(t)$

HWS \Rightarrow No even harmonics in Fourier series expansion

$$\Rightarrow i_1(t) = \sum_{n \rightarrow \text{odd}} I_{a_n} \cos n\omega t + \sum_{n \rightarrow \text{odd}} I_{b_n} \sin n\omega t$$

$$(\omega = 2\pi/T)$$

$$i_1(t) = I_{a_1} \cos \omega t + I_{b_1} \sin \omega t + I_{a_3} \cos 3\omega t + I_{b_3} \sin 3\omega t + \dots$$

$$i_{eq}(t) = I_a \cos \omega t + I_b \sin \omega t$$

$$V_1 = V_m \sin \omega t$$

$$\frac{1}{2\pi} \int V_1 i_1 dt = \frac{1}{2\pi} \int V_1 i_{eq} dt \rightarrow \text{same core loss}$$

$$\Rightarrow \frac{V_m I_{b_1}}{2} = \frac{V_m I_b}{2}$$

$$\Rightarrow I_{b_1} = I_b$$


I_{rms} is same (same wire loss)

$$\sqrt{I_{a_1}^2 + I_{b_1}^2 + I_{a_3}^2 + I_{b_3}^2 + \dots} = \sqrt{I_a^2 + I_b^2}$$

$$\Rightarrow I_a = \sqrt{I_{a_1}^2 + I_{a_3}^2 + I_{b_3}^2}$$



Now, $V_1 = V_m \sin \omega t$
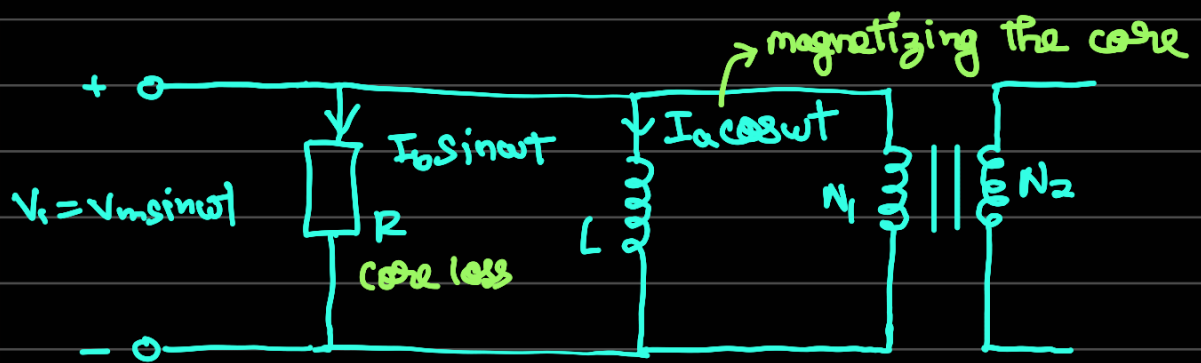
$$i_{eq} = I_a \cos \omega t + I_b \sin \omega t$$



→ Phasor diagram

(Assume anticlockwise rotation)

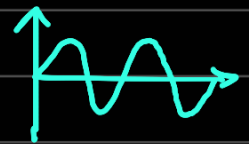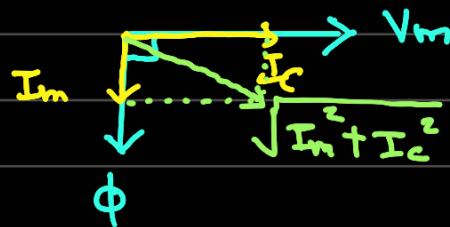


$$V_1(t) = V_m \sin \omega t$$

$$i_1(t) = I_a \cos \omega t + I_b \sin \omega t$$

$$P_{in}(t) = \underbrace{V_m I_a \cos \omega t \sin \omega t}_{\text{Reactive}} + \underbrace{V_m I_b \sin^2 \omega t}_{\text{Active}}$$

→ Transformer: with load

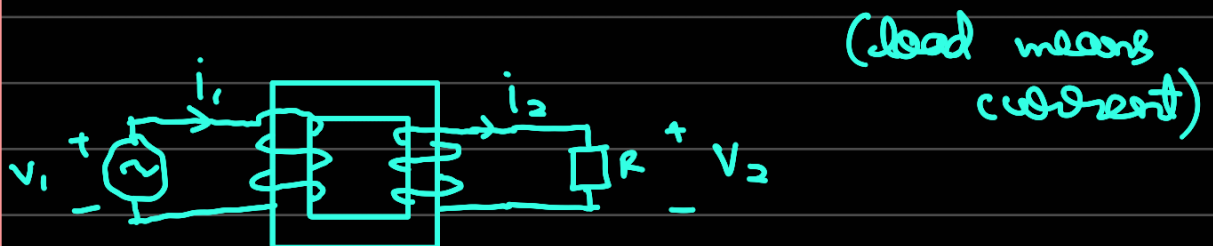

$$V_1 = \frac{d\psi_1}{dt} = N \frac{d\phi}{dt} \quad (\phi \text{ won't change})$$

★ Ideal transformer

- No core loss \Rightarrow loop area of hysteresis

core is zero

- Leakage effects of flux are neglected
- Resistance of wires is zero
- Core permeability is infinity

$$\left. \begin{aligned} v_1 &= N_1 \frac{d\phi}{dt} \\ v_2 &= N_2 \frac{d\phi}{dt} \end{aligned} \right\} \frac{v_1(t)}{v_2(t)} = \frac{N_1}{N_2}$$

$$\oint \vec{H} \cdot d\vec{l} = N_1 i_1 - N_2 i_2$$


$$\Rightarrow \frac{B \cdot l_c}{\mu_0 \mu_r} = N_1 i_1 - N_2 i_2 \quad (\text{no saturation effected})$$

$$\text{As } \mu_r \rightarrow \infty, \text{ LHS} = 0$$

$$\text{so } N_1 i_1 = N_2 i_2$$


$$\Rightarrow \frac{i_1}{i_2} = \frac{N_2}{N_1}$$
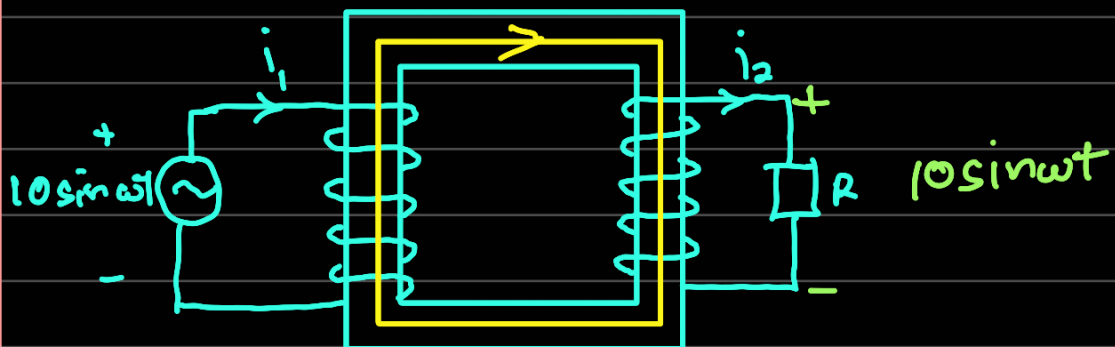
$$\text{so } v_1(t) i_1(t) = v_2(t) i_2(t)$$



①

Same sense of winding

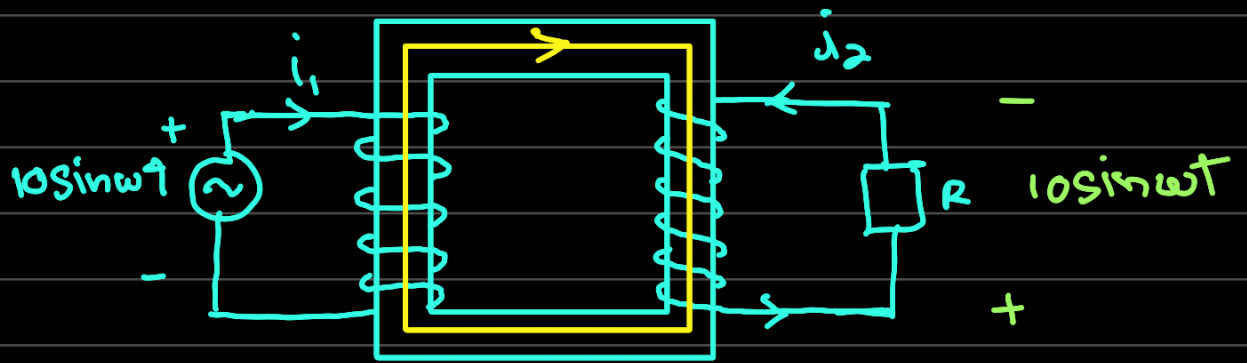

(2) Different sense of winding

→ Dot convention

