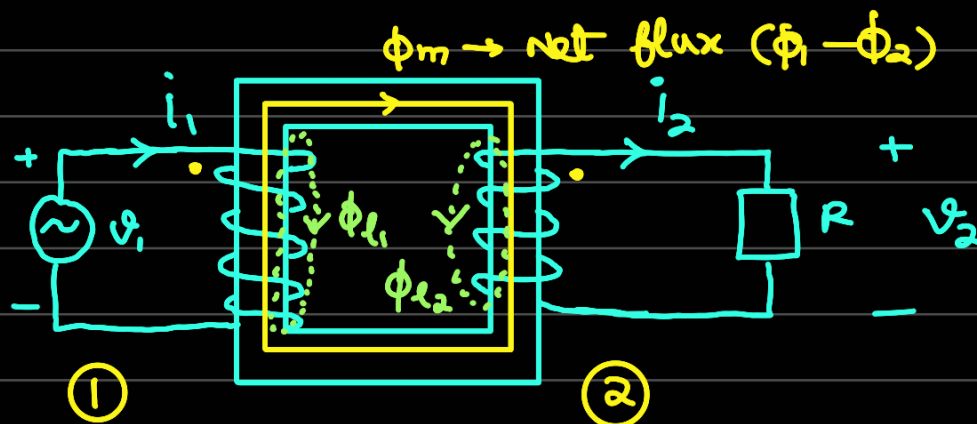


→ Transformer:



$$v_1 = i_1 R_1 + \frac{d\psi_1}{dt} \quad (R_1 \rightarrow \text{Resistance of primary winding})$$

Assumption \rightarrow lump model

$$\psi_1 = N_1 \phi_1 = N_1 (\phi_l + \phi_m)$$

$\phi_{l1} \rightarrow$ leakage flux (winding 1)

$\phi_{l2} \rightarrow$ leakage flux (winding 2)

$N_1 \phi_{l1} \rightarrow$ Assuming ϕ_{l1} passes all the windings, individual flux leakage for particular turns is neglected

$$\frac{d\psi_2}{dt} = i_2 R_2 + v_2$$

$$\psi_2 = N_2 \phi_2 = N_2 (\phi_m - \phi_{l2})$$

$$v_1 = i_1 R_1 + N_1 \frac{d\phi_{l1}}{dt} + N_1 \frac{d\phi_m}{dt}$$

Applying Ampere's circuital law (along path of ϕ_{l1})

$$\oint \vec{H} \cdot d\vec{l} = N_1 i_1 \quad (\text{LHS can't be simplified due to non-uniform path})$$

$$\Rightarrow \Phi_{l_1} \cdot R_{l_1} = N_1 i_1$$


→ equivalent reluctance for leakage flux Φ_{l_1}

$$\text{So } V_1 = i_1 R_1 + \frac{d}{dt} \left(\frac{N_1 i_1}{R_{l_1}} \right) + N_1 \frac{d\Phi_m}{dt}$$

$R_{l_1} \rightarrow$ constant (most of it is air)

$$V_1 = i_1 R_1 + \underbrace{\frac{N_1^2}{R_{l_1}} \frac{di_1}{dt}}_{L_{l_1}} + N_1 \frac{d\Phi_m}{dt}$$
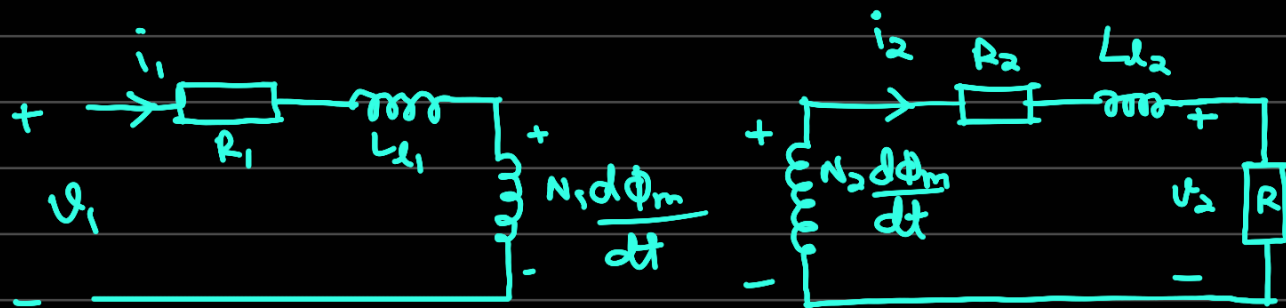
$$\Rightarrow V_1 = i_1 R_1 + L_{l_1} \frac{di_1}{dt} + N_1 \frac{d\Phi_m}{dt}$$



If secondary winding is wound on primary winding, leakage flux $\rightarrow 0$

Apply ACL along path of Φ_m .

$$\oint \vec{H} \cdot d\vec{l} = N_1 i_1 - N_2 i_2$$

$$\Rightarrow H_c l_c = N_1 i_1 - N_2 i_2$$

→ Assumed uniform

$$\Rightarrow \frac{B_c l_c}{\mu_0 \mu_r} = N_1 i_1 - N_2 i_2$$

all confined to core


Assumed $\mu_r \rightarrow \text{constant}$
 $B \text{ vs } H \rightarrow \text{linear}$ \rightarrow
 NO saturation NO core loss

$$\Rightarrow \frac{\Phi_m l_c}{\mu_0 \mu_r A_c} = N_1 i_1 - N_2 i_2$$

$$\Rightarrow \Phi_m R_c = N_1 i_1 - N_2 i_2$$

[For ideal transformer, $\mu_r \rightarrow \infty$
 $\Rightarrow R_c \rightarrow 0$]
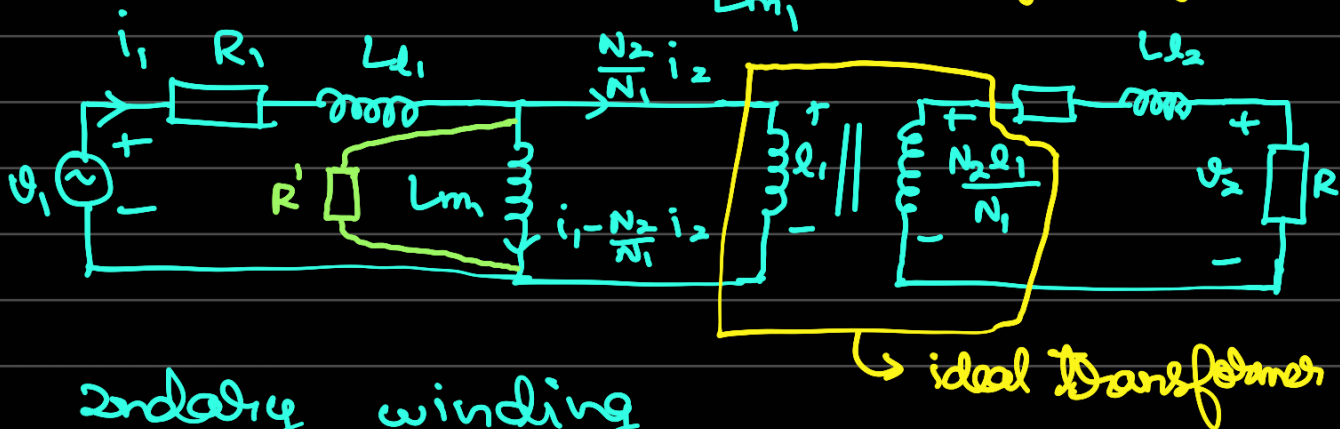
$$\begin{aligned} V_1 &= i_1 R_1 + L_{l1} \frac{di_1}{dt} + N_1 \frac{d}{dt} \left(\frac{N_1 i_1 - N_2 i_2}{R_c} \right) \\ &= i_1 R_1 + L_{l1} \frac{di_1}{dt} + \underbrace{\frac{N_1^2}{R_c}}_{L_{m1}} \frac{d}{dt} \underbrace{\left(i_1 - \frac{N_2}{N_1} i_2 \right)}_{\text{magnetising current}} \end{aligned}$$



secondary winding

$$-N_2 \frac{d\Phi_{l2}}{dt} + N_2 \frac{d\Phi_m}{dt} = i_2 R_2 + V_2$$

$$\Rightarrow N_2 \frac{d\Phi_m}{dt} = i_2 R_2 + L_{l2} \frac{di_2}{dt} + V_2$$

$R' \rightarrow$ for core loss