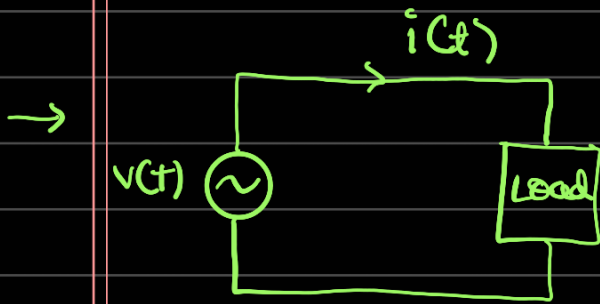


## Day - 9



$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = i_m \cos(\omega t + \theta_i)$$

$$\text{So } P = v i = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$+ \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)}_{\text{Becomes 0 over a cycle}}$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$


$$= \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_{\text{Useful power}}$$

$$S = VI \quad (\text{Apparent; VA})$$

$$P = VI \cos \theta \quad (\text{Real; W})$$

$$Q = VI \sin \theta \quad (\text{Reactive; VAR})$$

$$S = \sqrt{P^2 + Q^2} \equiv S \pm jQ$$

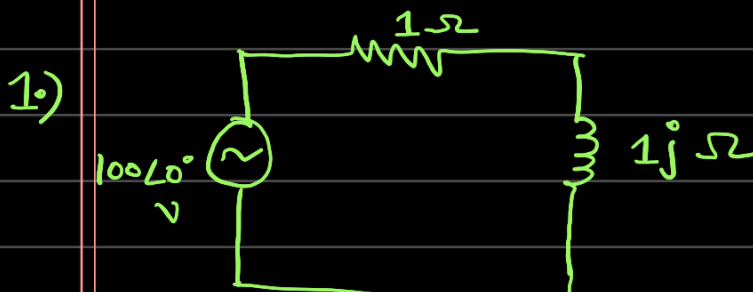

Find  $S, P, Q$   
(100 → RMS)

Ans) 
$$I_{rms} = \frac{100}{1+j}$$

So 
$$S = VI = 100^2$$

$$= 5000(1-j)^*$$

$$\text{so } P = 5 \text{ kW}$$

$$Q = 5 \text{ kVA}_r$$

$$S = 5\sqrt{2} \text{ kVA}$$

\* we do  $VI^*$  to preserve sign convention ( $P_L > 0$ ,  $P_C < 0$ )

→ Power Factor is the cosine of angle between voltage and current vectors. It is also the ratio of active power and apparent power.

→ Power Factor is the property of the load.

2.) Replace  $1j \Omega$  with  $4j \Omega$ ;  $1\Omega$  with  $3\Omega$ . Do the same things.

$$\text{Ans.) } \vec{I} = \frac{100}{3+4j} = 4(3-4j) = 20 \angle -53.13^\circ$$

$$\vec{V} = 100 \angle 0^\circ$$

$$\vec{S} = \vec{V} \cdot \vec{I}^* = 100 \angle 0^\circ \times 20 \angle 53.13^\circ = 100 \times (12 + 16j)$$

$$= 1200 + 1600j \text{ VA}$$

3.)



Find  $S$

Ans.)

$$Z = 4 - 2j = 2\sqrt{5} \angle -26.57^\circ \Omega$$

$$I = \frac{5 \angle 30^\circ}{2\sqrt{5} \angle -26.57^\circ}$$

$$= \frac{\sqrt{5}}{2} \angle 56.57^\circ \text{ A}$$

$$S = VI^*$$
$$= 5 \angle 30^\circ \frac{\sqrt{5}}{2} \angle -56.57^\circ$$

$$= \frac{5\sqrt{5}}{2} \angle -26.57^\circ \text{ VA}$$

→ MPTT-



$$Z_L = Z_{Th}^*$$

max. power gets transferred from source to load when load impedance = complex conjugate of source impedance.

4.)



Find  $R_L$  for MPT

Ans.)

$$Z_{Th} = \frac{(40 - 30j) 20j}{40 - 10j}$$

$$= 9.41 + 22.35j$$

$$\text{so } R_L = |Z_{Th}| = 24.25 \, \Omega$$

