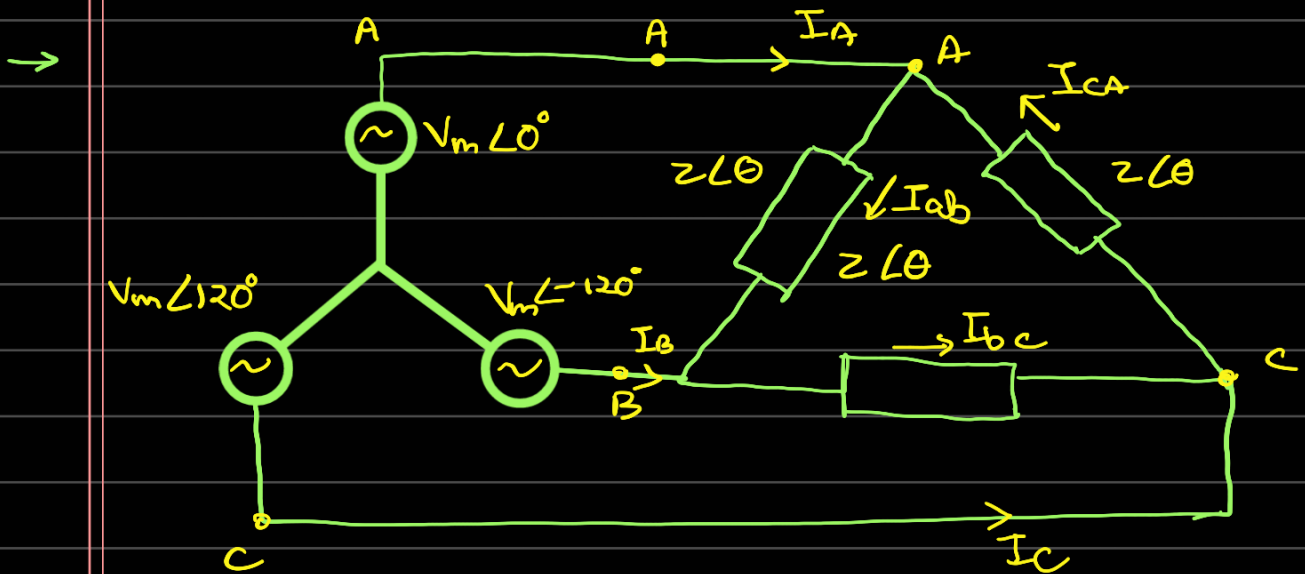


Day-11



$$V_{an} = V_m \sin \omega t$$

$$V_{bn} = V_m \sin(\omega t - 120^\circ)$$

$$V_{cn} = V_m \sin(\omega t + 120^\circ)$$

↓
peak

$$V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_m \sin(\omega t + 30^\circ)$$

$$V_{bc} = \sqrt{3} V_m \sin(\omega t - 90^\circ) = V_{ab} \angle -120^\circ$$

$$V_{ca} = \sqrt{3} V_m \sin(\omega t + 150^\circ) = V_{ab} \angle 120^\circ$$


$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$


$$I_A = \sqrt{3} I_{ab} \angle -30^\circ$$

$$I_{ca} = I_{ab} \angle 120^\circ$$


$$\text{so } I_A = I_{ab} - I_{ca}$$

$$= \sqrt{3} I_{ab} \angle -30^\circ$$

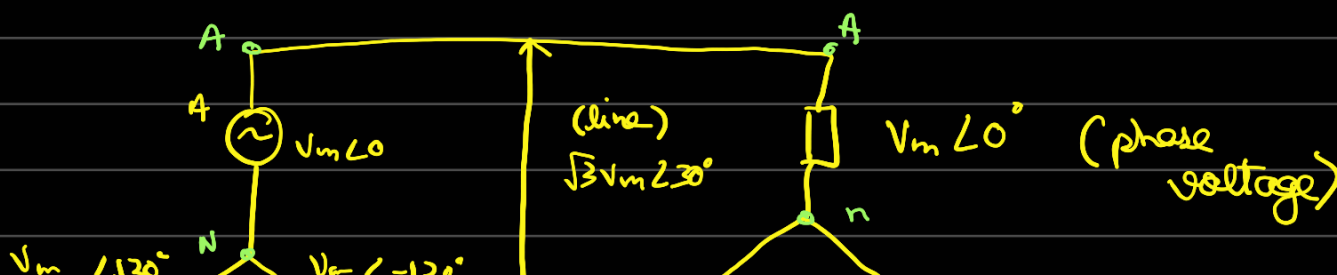

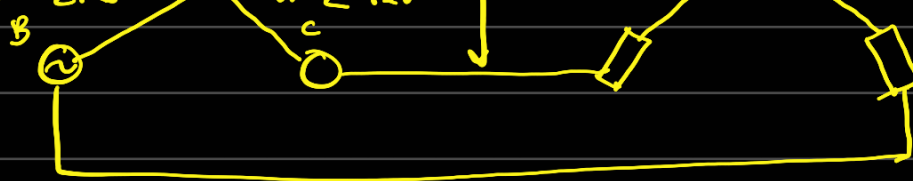

1.)

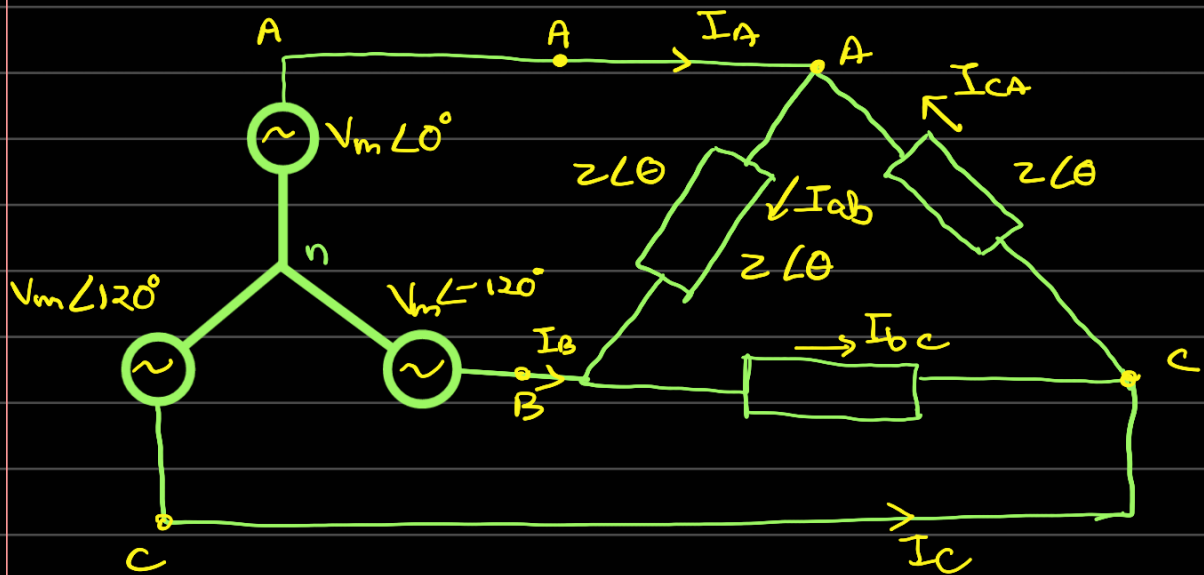

$$V_{an} = 100 \angle 0^\circ$$

$$Z = 8 + 4j$$

Find I_{ab} , I_{bc} , I_{ca} ,
 I_a , I_b , I_c

Ans)
$$I_{ab} = \frac{\sqrt{3} V_{an} \angle 30^\circ}{4\sqrt{5} \angle 26.565^\circ}$$

$$= 25 \sqrt{\frac{3}{5}} \angle 3.435^\circ$$

$$= 19.365 \angle 3.435^\circ \text{ A}$$

$$I_{bc} = I_{ab} \angle -120^\circ$$

$$= 19.365 \angle -116.565^\circ \text{ A}$$

$$I_{ca} = I_{ab} \angle 120^\circ$$

$$= 19.365 \angle 123.435^\circ$$


$$I_a = \sqrt{3} I_{ab} \angle -30^\circ$$

$$= 33.541 \angle -27.565^\circ \text{ A}$$

$$I_b = \sqrt{3} I_{bc} \angle -30^\circ = 33.541 \angle -146.565^\circ$$

$$I_c = \sqrt{3} I_{ca} \angle -30^\circ = 33.541 \angle 93.435^\circ$$

2.)

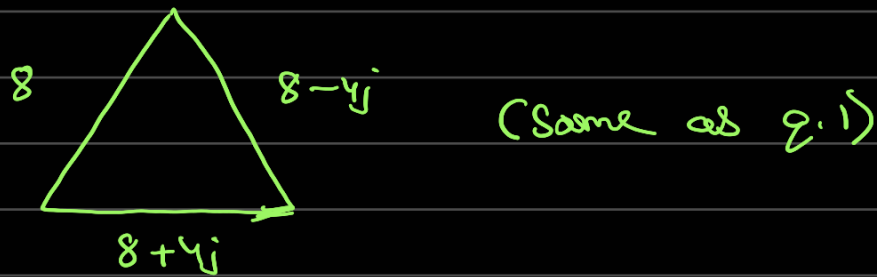

$$I_{AB} = \frac{100\sqrt{3}}{8} \angle 30^\circ = 21.65 \angle 30^\circ$$


$$I_{BC} = \frac{100\sqrt{3}}{8+4j} \angle -90^\circ = 19.365 \angle -116.565^\circ$$

$$I_{CA} = \frac{100\sqrt{3}}{8-4j} \angle 150^\circ = 19.365 \angle 176.565^\circ$$


$$I_A = I_{AB} - I_{CA}$$

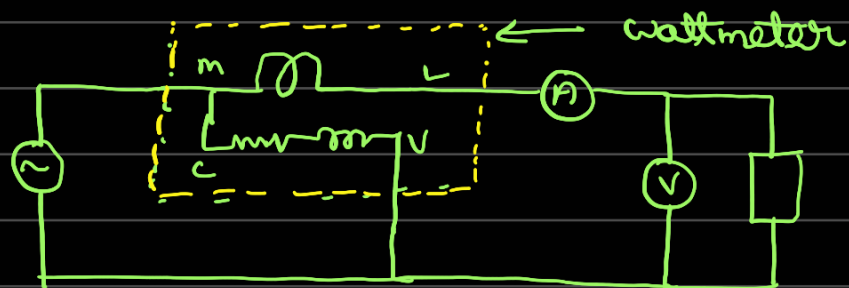3.) (H.W.)

2 wattmeters are sufficient to measure 3-phase power in a circuit. Explain how.



→ 3-phase power:

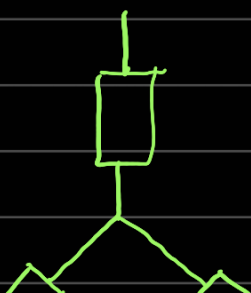


$$P = 3V_p I_L \cos \theta$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta$$



$$= \sqrt{3} V_L I_L \cos \theta$$

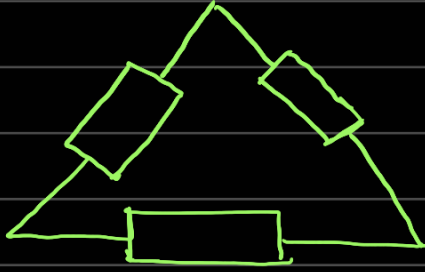

$$P = 3 V_L \frac{I_L}{\sqrt{3}} \cos \theta$$

$$= \sqrt{3} V_L I_L \cos \theta$$

Active power in 3-phase circuit is $\sqrt{3} V_L I_L \cos \theta$


$$P = \sqrt{3} V_L I_L \cos \theta$$

$$Q = \sqrt{3} V_L I_L \sin \theta$$

$$S = \sqrt{3} V_L I_L$$

- 4.) Each transmission line of 3-wire 3-phase system has $Z = 15 + 20j \Omega$. System delivers $P_{\text{total}} = 160$ kW at 12 kV to a balanced 3-phase star connected load with a lagging p.f. = 0.86.

- Determine $|V_{AB}|$
- Find p.f. of total load as seen by source.
- Efficiency of transmission?

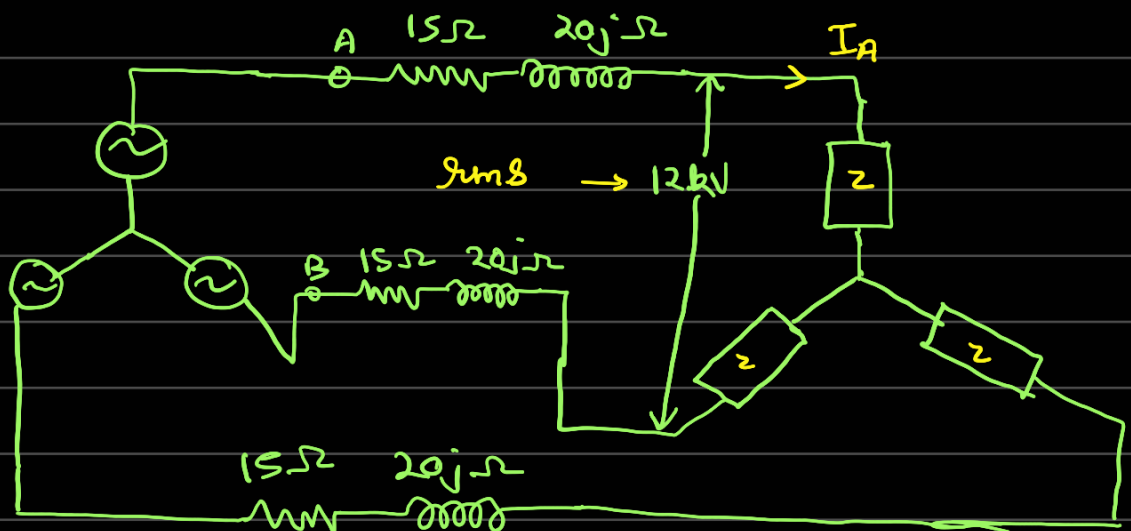

Ans) a.) $I_A (\text{rms}) = \frac{160/3}{\sqrt{3} \times 0.86} = 8.95 \text{ A}$

$$Z = \frac{12/\sqrt{3}}{8.95} \angle -\cos^{-1} 0.86 \times 1000 \Omega$$

$$= 774.1 \angle -30.68^\circ \Omega$$

$$Z_T = 774.1 \angle -30.68 + 25 \angle 53.13^\circ$$

$$= 680.726 - 375.019j$$

$$= 777.19 \angle -28.85^\circ$$

$$|V_{AB}| = \sqrt{3} \times 8.95 \times 777.19 \times 10^{-3} \text{ kV (rms)}$$

$$= 12.05 \text{ kV}$$

b.) $P.f. (Total) = \cos(-28.85^\circ) = 0.876$

c.) $Efficiency = \frac{160}{\sqrt{3} \times 12.05 \times 8.95 \times 0.876} = 0.9778$
 $\approx 97.78\%$

